

OLLSCOIL NA hÉIREANN, GAILLIMH
NATIONAL UNIVERSITY OF IRELAND, GALWAY

SEMESTER II EXAMINATIONS 2000/2001



THIRD YEAR ELECTRONIC ENGINEERING
THIRD YEAR ELECTRONIC AND COMPUTER ENGINEERING

EE321 ANALOGUE SYSTEMS DESIGN II

Professor L.E. Davis
Professor D.J. Wilcox
Mr. J. Breslin

Duration of Examination: **TWO** hours
Instructions: Answer **THREE** questions

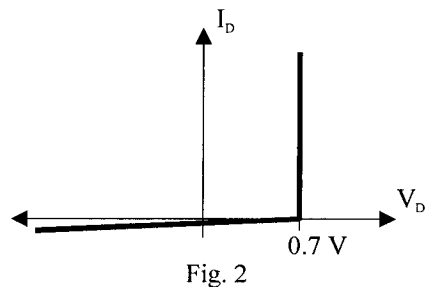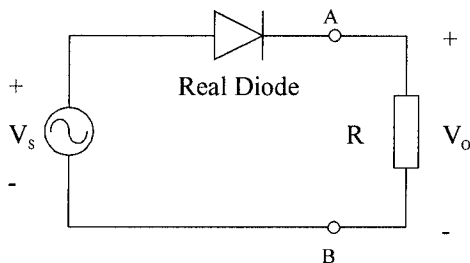- 1.
- (a) Draw a simple model for the real diode. [1 mark]
 - (b) What is the purpose of the circuit in Fig. 1? [2 marks]
 - (c) For a sinusoidal input waveform V_s with a peak-to-peak voltage of 5 V, sketch the output waveform V_o if the characteristic curve of the real diode is as shown in Fig. 2. [4 marks]
 - (d) Describe the effect on V_o of placing a capacitor C in parallel with the load, i.e. between points A and B in the circuit. [4 marks]
 - (e) Give an expression for the percentage ripple on the output signal V_o when the capacitor is included in the circuit. [4 marks]
 - (f) Calculate the percentage ripple if the circuit parameters are as follows: the period of the input sinusoidal waveform is 16.7 ms, the input peak-to-peak voltage is 5 V, the load resistance is 100Ω , and the capacitor value is $1000 \mu\text{F}$. What would happen if C were increased? [5 marks]



[cont'd]

2.

(a) Write a short description for any three of the following types of diode. [3 x 3 marks]

- Schottky diode
- Varactor diode
- LED
- Flyback diode
- Photo diode

(b) A Zener diode circuit for voltage regulation is given in Fig. 3.

- (i) Sketch the i_D vs. v_D characteristic for a Zener diode showing the various regions of operation. [2 marks]
- (ii) In which region does the Zener diode operate for the voltage regulator application shown? [1 mark]
- (iii) For varying source voltage and load current, analyse the circuit in Fig. 3 to determine the proper range of values for R_i that will allow the diode to maintain a constant output voltage (by keeping the Zener current between its minimum and maximum values). [6 marks]
- (iv) Define percentage regulation for the Zener diode voltage regulator. [2 marks]

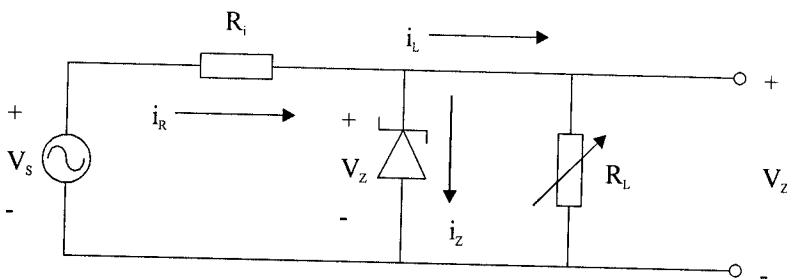


Fig. 3

3.

- (a) What is meant by the term “common emitter”? [1 mark]
- (b) Perform a DC analysis of the base biasing section of the common emitter amplifier as shown in Fig. 4, and hence derive formulæ for the position of the DC operating point. [8 marks]
- (c) Calculate the DC operating point for this common emitter amplifier circuit with the component values given in Table 1. [6 marks]
- (d) Find the value of I_B , i.e. the i_b characteristic on which the DC operating point lies. [2 marks]
- (e) What is the equation of the DC load line for this common emitter amplifier circuit? [3 marks]

$V_{CC} = 30 \text{ V}$	$R_E = 2.2 \text{ k}\Omega$
$R_{B1} = 33 \text{ k}\Omega$	$R_C = 10 \text{ k}\Omega$
$R_{B2} = 4.7 \text{ k}\Omega$	BJT $\beta = 75$

Table 1

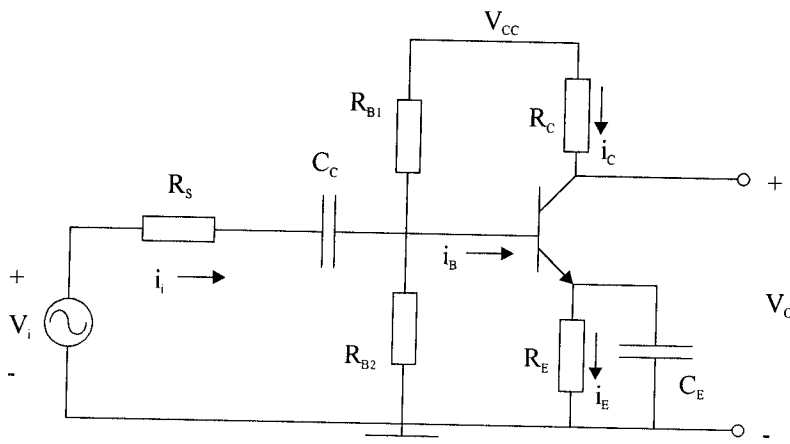


Fig. 4

[cont'd]

